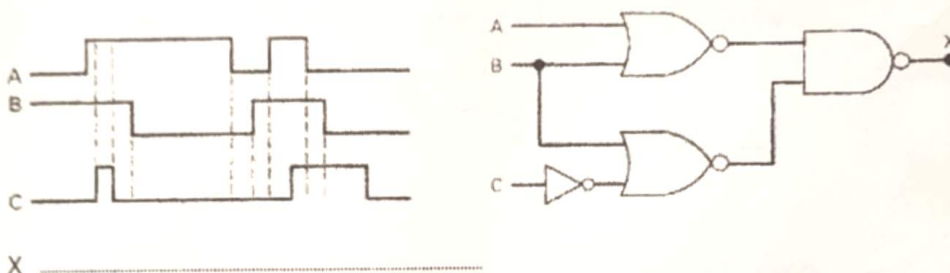


Exam of Combinational and Sequential Logic

Exercise 1: *The questions of this exercise are not related, so you can start by anyone you want*

- 3 pts 1. Do: $A2B - 8AC = ?$ $(48,75)_{dec} = (?)_{hex}$ $(10110010)_{gray} = (?)_{hex}$
- 2,5 2. Given the 8-bit data word, 01011011, generate the 12-bit word of the Hamming code.
- 3 pts 3. Use a SR flip-flop to construct a T flip-flop, and deduce how to use SR on toggle mode.
- 2 pts 4. Give the expression of the output X , of the following circuit, and complete the waveform of the output X in the Figure.




Exercise 2: 4 pts

Implement the logic expression $F = AB + \bar{B}C$ using:

- 3 to 8 decoder and an OR gate.
- an 8-to-1 multiplexer
- a 4-to-1 multiplexer

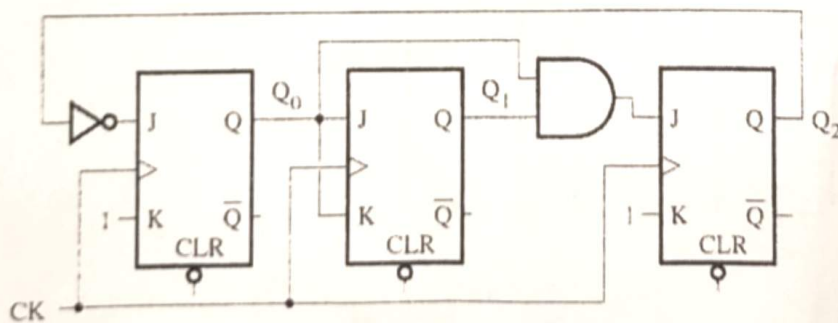Exercise 3: 6 pts

Consider the counter shown in Figure, whose flip-flops are initially set to 0:



1. Determine the logic equations for the J and K inputs of each flip-flop.
2. Give the transition table of JK flipflop and complete the transition table of the counter.
3. Construct the state diagram (cycle of the counter).
4. Deduce the counter modulo.

Good Luck!